

Test #1: EE 253 Electronics I FS13  
September 13, 2013

40


1) Multiple Choice Questions (40 points, no partial credits)

A 1.1) How many valence electrons do acceptor impurity atoms have, which are doped into Silicon?  
a) 3; b) 4; c) 5; d) 6

C 1.2) What is a doping process?  
a) A process to break covalent bonds;  
b) A process to cause avalanche;  
c) A process to improve carrier concentrations;  
d) A process to create holes

B 1.3) The built-in voltage in a stand-alone PN junction is initially caused by  
a) Drift; b) Diffusion; c) Breakdown; d) Doping

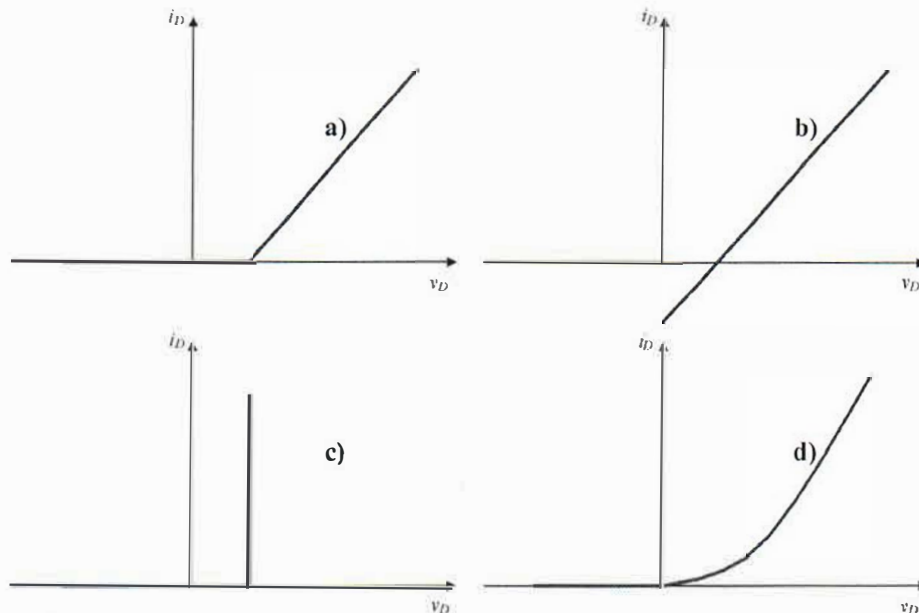
C 1.4) Two diodes that have different turn-on voltage values are in parallel to form a current divider. Which of the following model could be used as a diode model, but is NOT suitable to analyze the current distribution between the two diodes in this case?



A 1.5) Thermal voltage  $V_T$  is approximately  
a) 26 mV @ 300K; b) 26 mV @ any temperature;  
c) 26 mV @ 300°F; d) 26 mV @ 300°C

D

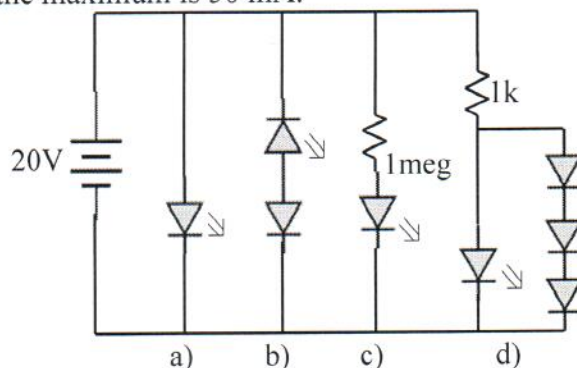- 1.6) Which of the following LED is on? Assume  $V_{y,LED} = 2V$ ,  $r_{f,LED} = 20\Omega$  for LEDs, and  $V_y = 0.7V$ ,  $r_f = 0$  for all other diodes. Suppose the minimum LED current is 0.1 mA, and the maximum is 50 mA.



$$\frac{20 - 2}{20}$$

$$\begin{array}{c} + \\ 1V \\ - \end{array} \quad \begin{array}{c} \downarrow 10mA \\ \text{diode symbol} \end{array}$$

D

- 1.7) A diode is biased in the "ON" region,  $V_y$  is unknown, and  $r_f = 2\Omega$ . The voltage across the diode ( $V_D$ ) is 1 V when the current flowing through it ( $I_D$ ) is 10 mA. If  $I_D$  changes to 20mA, what is  $V_D$  now?  
a) 1.04 V; b) 1.0 V; c) 0.98 V; d) 1.02 V

B

- 1.8) For a reverse-biased PN junction (not biased in the breakdown region),  
a) its depletion region is narrowed;  
b) there's a leakage current which is often extremely small  
c) current increases with voltage exponentially;  
d) it can be modeled with a voltage source and a forward resistance


$$V_D = 1.02$$

$$V_D = 0.98V$$

$$\begin{array}{c} + \\ 1V \\ - \end{array} \quad \begin{array}{c} \frac{1}{20} V_D \\ \frac{1}{20} \end{array}$$

2) In the following diode circuit,

34

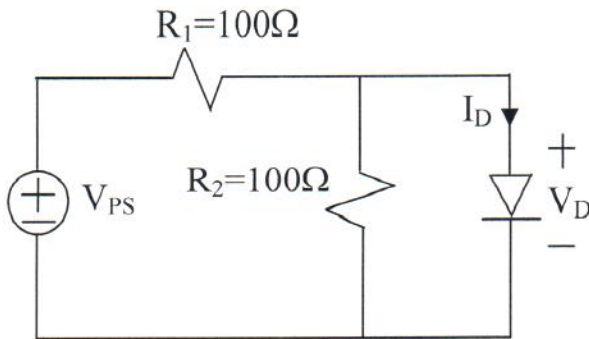

a) (20 points): if  $V_{PS} = 1.0 \text{ V}$ ,  $V_\gamma = 0.7 \text{ V}$  and  $r_f = 0 \text{ Ohms}$ , what are the diode current  $I_D$ , the diode voltage  $V_D$ , and the dissipated power  $P_D$  in the diode?

$$V_{PS} - R_1 \left( I_D + \frac{V_D}{R_2} \right) - V_D = 0 \rightarrow \boxed{\text{If on}}$$

$$1 = 100 \left( I_D + \frac{.7}{100} \right) + .7$$

$$.3 = 100 I_D + .7 \quad \times$$



$$\begin{matrix} I_D < 0 \\ \rightarrow \text{Diode off} \end{matrix} \rightarrow V_D = V_{R_2} = V_{PS} \frac{100}{100+100} = .5 \text{ V} < .7 \text{ V}$$

$$\boxed{V_D = .5 \text{ V}} \\ \boxed{I_D \approx 0 \text{ A}}$$

$$P_D = ? \quad -3$$

b) (20 points): if  $V_{PS} = 6.6 \text{ V}$ ,  $V_\gamma = 0.7 \text{ V}$  and  $r_f = 2 \text{ Ohms}$ , what are the diode current  $I_D$ , the diode voltage  $V_D$ , and the dissipated power  $P_D$  in the diode?

$$V_{PS} = R_1 \left( I_D + \frac{V_D}{R_2} \right) + V_D$$

$$V_D = V_\gamma + I_D r_f = .7 + 2 I_D$$

$$6.6 = 100 \left( I_D + \frac{.7 + 2 I_D}{100} \right) + .7 + 2 I_D$$

$$6.6 = 100 I_D + .7 + 2 I_D + .7 + 2 I_D$$

$$5.2 = 104 I_D$$



$$\boxed{I_D = 50 \text{ mA}}$$

$$\boxed{V_D = .8 \text{ V}}$$


$$V_D = V_\gamma + 2 I_D = .7 + 2(.05)$$

$$P_D = ? \quad -3$$

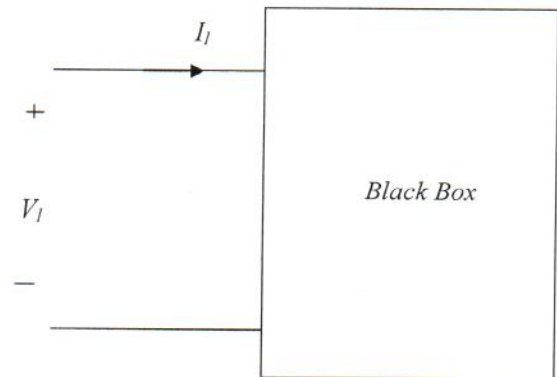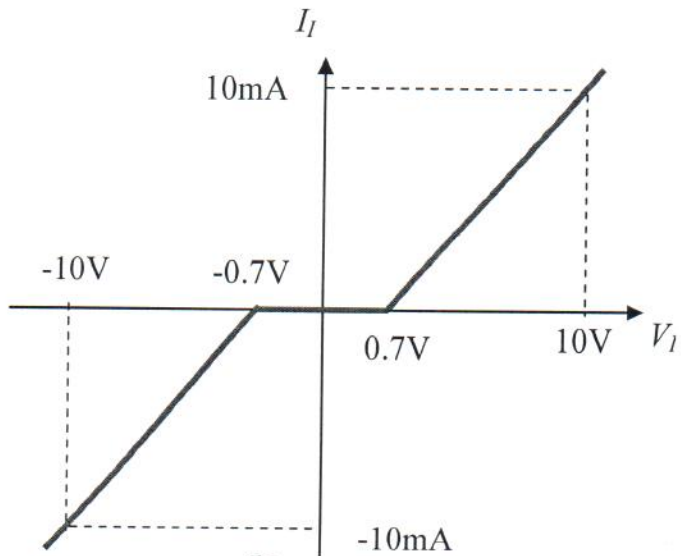- 20  
3) (20 points) Design a circuit using diodes and resistors to produce the following  $I_I$ - $V_I$  characteristics, where  $I_I$  and  $V_I$  are the input current and voltage to the overall circuit. Use the ideal diode model with  $V_\gamma = 0.7\text{V}$  and  $r_f = 0$ . Please calculate resistor values.



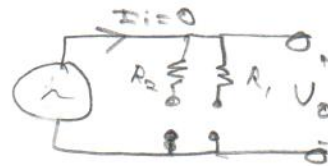Diodes off  
 $-0.7\text{V} \leq V_I \leq 0.7\text{V}$   $I_I = 0$



$$V_I = R_1 I_I + V_\gamma$$

$$R_1 = \frac{V_I - V_\gamma}{I_I} = \frac{10 - 0.7}{10\text{mA}}$$

$$R_1 = 930\Omega$$

$$R_1 = R_2$$

$$R_2 = \frac{-10 + 0.7}{-10\text{mA}}$$

$$R_2 = 930\Omega$$